

Procedure : 1) First we open the circuit maker application in our device.

2) Then we click on the device option on the upper menu-bar and then click on browse. We search digital basics option to get the desired logic gates required, i.e., here we need 2 XOR gate, 2 AND gate, 2 NOT gate and 1 OR gate.

3) For input, we browse for switches in the device option and copy as many switches we need here.

4) For output, we browse the logic display option and place the LEDs on our screen

5) Then we connect all the gates with switches and LED with the help of \oplus button to see the circuit.

6) Lastly, we click on the run button to see the circuit running and verify our truth table.

Conclusion : This experiment includes the design and implementation of half and full subtractor and also full subtractor using half subtractors

This experiment enhanced our knowledge of circuit design and to perform arithmetic operation

Cur 19/8/23

Half Address:

Definition: Half adder is a combinational logic circuit that is designed to add two binary digits. The half adder produces the output along with a carry (if any). The half adder adds the circuit can be designed by connecting an XOR gate and an AND gate. If it has two input terminals and two output terminals for sum (s) and carry (c).

The output of the XOR gate is the sum of two bits and the output of the AND gate is carry bit.


Truth Table:

Inputs	Outputs	A	B	Sum (carry)
0 0	0 0	0	0	0
0 1	1 0	0	1	1
1 0	0 1	1	0	1
1 1	1 1	1	1	0

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = A \cdot B$$

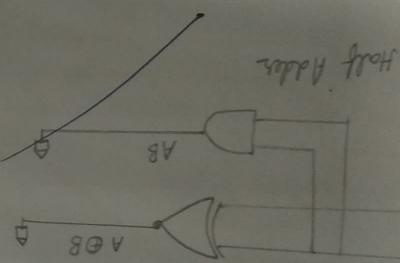Experiment - 4
Design a half adder, full adder and also full adder using 2 half adders using circuit model (VLSI).



Procedure: i) First we open the circuit maker application in your device.

ii) Then click on the device option on the upper menu bar and click on browse. We search digital basics option to get the desired logic gates required, i.e., here we need one XOR gate and one AND gate.

iii) For input we browse for switches in the device option and place as many as required.

iv) For output we browse the logic display option and place the LEDs on our screen.

v) Then we connect all the gate with the switches and LED with the help of \oplus button to see the complete circuit.

vi) Lastly, we click on the run button to see the circuit working and then verify the truth table.

$$\text{Carry} = AB + BC + AC$$


$$Sum = ABCD$$

	1	1	1	1	1	1	1
	1	0	0	1	1	0	1
	1	0	1	0	1	0	0
	0	1	0	0	1	1	0
	1	0	1	1	0	0	1
	0	1	0	1	1	0	0
	0	0	1	1	1	0	0
	0	0	0	0	0	1	0
A	0	B	0	C	0	Sum	Carry
Input	1	Output	1	Output	1	Output	1


Bubble node

The full adder consists of one XOR gate, three AND gates and one OR gate.

Full Adder:

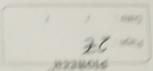

Full Adder

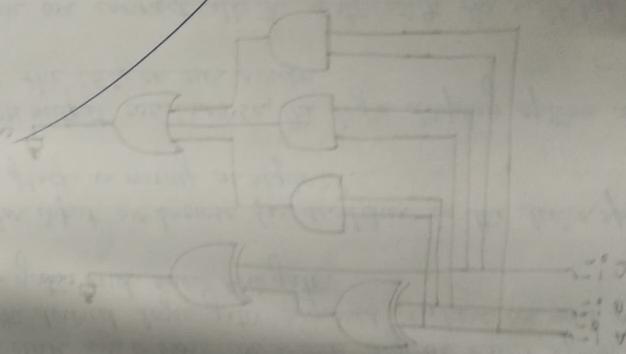

Procedure: i) First we open the circuit maker application in your device.

ii) Then we click on the device option on the upper menu bar and click on the browse. We search digital basics option to get the desired logic gates, i.e., here we need one XOR gate, 3 AND gates and one OR gate.

iii) For input, we browse for switches in the device option and place many as required

iv) For output, we browse for digital logic display options and click on LEDs and place them.

v) Then we connect all the gates with the switches and LED with the help of \oplus button to see the complete circuit.

vi) Lastly, we click on the run button to see the circuit working and then verify the truth table.

Full Adder using 2 Half Adders


Theory: To build a full adder, you need two half adders. One half adder is used, to add the two input bits (A and B) while the other half adder combines the sum output of first half adder with the third input to produce the final sum output and Carry Output.

This way we can create a full adder by cascading 2 half adders.

Using half adders to construct full adder provides not only modularity but also reusability. A half adder is a basic block that adds two input bits. By combining multiple half adders, you can construct larger adders with ease. This approach simplifies the design of the circuit.

Procedure: i) First we open the circuit maker application in our device.

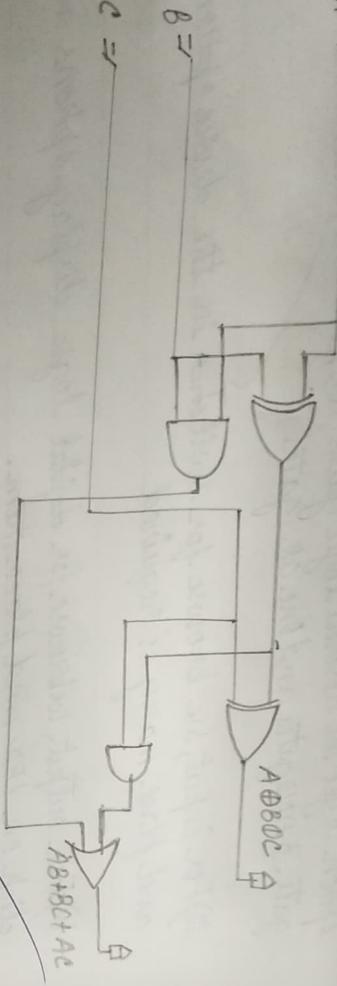- When we click on the device option on the upper menu bar and click on browse, it search digital logic open



Full Adder using 2 Half Adders

to get the desired logic gates, i.e., here we need 2 XOR gate
2 AND gate and OR gate.

iii) For input, we browse for switches in the device option and place as many required

iv) For output, we browse the logic display option and place the LEDs on our board.


9) Then we connect all the gate with the switches and LED which with the help of \oplus button is joined, to see the complete circuit.

vii) Lastly, we click on the run button to see the circuit working and then verify the truth table.

Conclusion: This experiment includes the design and implementation of half adder, full adder, and also full adder using half adders.

This experiment enhanced our knowledge of circuit design and to perform arithmetic operation.

~~Curves~~

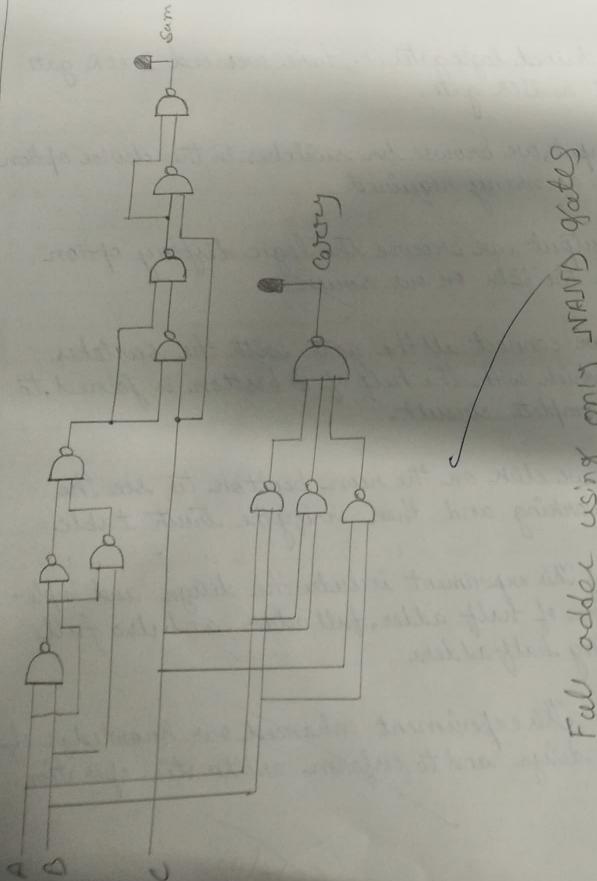

Experiment-5
Topic : Design a full adder using only NAND gates.

PIONEER®

Page 31

Date / /

Theory: Full Adder is a combinational logic circuit which performs binary addition on three binary bits.

NAND gates are universal gates as any logic system can be implemented using these two gate. The full adder circuit can also be implemented using NAND gates and sum (S) and carry (C) function is:

$$S = (A \oplus B) \cdot (A \oplus B)C + C \cdot (A \oplus B)C$$

$$C = \overline{C \cdot (A \oplus B) \cdot \overline{AB}} = AB + (A \oplus B)C = AB + BC + AC$$


Truth Table of Full Adder :

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Procedure:

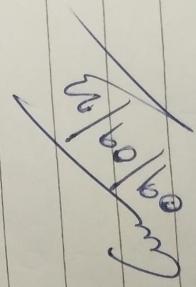- i) Open Circuit maker and create a new project
- ii) Then click on the device option on the upper menu bar and click on browse. We search digital basics option to get the desired logic gates required, i.e., here we need only ~~NAND~~ NAND gates.
- iii) For input we browse for switches in the device option and place as many as required.
- iv) For output, we browse the logic display option
- v) For output, we browse the logic display option and place the LEDs; here we need two LEDs.
- vi) Then we connect the gates with the switches and LEDs with the help of \oplus button to see the complete circuit.
- vii) Lastly, we click on the run button to see the circuit working and then verify our truth table.

Conclusion: Here, we get to learn about the working of the full adder which is made using only NAND gates and also its respective circuit diagram.



Experiment - 6

Topic: Design a 4-bit parallel adder using
circuit maker v6.

DIGICCA®

Page: 33
Date: 09/09/23

Theory: A 4-bit parallel adder is a digital circuit that can add two 4-bit binary numbers in parallel. It consists of 4 full-adder circuits, each responsible for adding one bit of the numbers. The carry-out from one full adder is connected to the carry-in bit of the next. The common 4-bit parallel adder IC is 74LS83 which combines full-adder circuits into a single package.

Using Input: $A_4 A_3 A_2 A_1$ $B_4 B_3 B_2 B_1$
 1101 , 1011

C_{in} is always initialised 0.
calculations

→

	$c=1$	$c=1$	$c=1$	$c=1$	$(C_{in}=0)$
1	1	0	1	1	
1	0	1	0	0	
1	1	0	0	0	
$(C_{out} \text{ } AX)$	1	1	0	0	
	↓	↓	↓	↓	
	S_1	S_3	S_2	S_1	

Truth Table :

<u>Input (A)</u>	<u>Input (B)</u>	<u>Output(s)</u>	<u>Carry</u>
$A_4 = 1$	$B_1 = 1$	$S_2 = 1$	$C_{out} = 1$
$A_3 = 1$	$B_2 = 0$	$S_2 = 0$	$C_3 = 1$
$A_2 = 0$	$B_2 = 1$	$S_2 = 0$	$C_2 = 1$
$A_1 = 1$	$B_1 = 1$	$S_1 = 0$	$C_{10} = 1$
			$C_m = 0$

Procedure : i) Firstly we open the circuit maker (v6) application on our device.

ii) Then we go on menu and then click on "deviceoption" and then find the 4-bit parallel adder whose common re is 74LS83 and place it on our screen.

iii) For inputs, we go to browser option and then select switches for input A, input B and one carry input.

iv) For outputs, we go to display logics option and then here are need 5 LEDs \rightarrow 4 sum output and 1 for Cout.

v) Then we connect all the switches and LEDs to the re of 4-bit parallel adder and click on run to

Topic :

PRACTICAL

Page 25

Date : / /

Check the proper working of the circuit and verify the truth table.

Conclusion: By doing this experiment about 1-bit parallel adder we can also do 2 bit or 1 bit binary addition and verify the respective truth table.

Experiment - 7

Design a 16-bit parallel adder using
circuit maker (4)

Date: 09/09/23
Page: 36

Theory: A 16-bit parallel adder is a circuit that can add two 16-bit binary numbers together. It does this by performing binary addition on each pair of corresponding bits and propagating any carry generated from one bit to another bit. A 16-bit parallel adder is made here using 4 4-bit parallel adder.

Using inputs:

A_{16}	A_{15}	A_{14}	A_{13}	A_{12}	A_{11}	A_{10}	A_9	A_8	A_7	A_6	A_5	A_4	A_3	A_2	A_1	
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1
1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
B_4	B_5	B_4	B_3	B_2	B_1	B_0	S_9	S_8	S_7	S_6	S_5	S_4	S_3	S_2	S_1	S_0
1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
S_5	S_4	S_3	S_2	S_1	S_0	C_9	S_9	S_8	S_7	S_6	S_5	S_4	S_3	S_2	S_1	S_0

Truth Table

Input (A)	Input (B)	Output (S)	Carry (C)
$A_{16} = 0$	$B_{16} = 1$	$S_{16} = 1$	$C_{16} = 0$
$A_{15} = 0$	$B_{15} = 0$	$S_{15} = 0$	$C_{15} = 0$
$A_4 = 0$	$B_4 = 0$	$S_4 = 0$	$C_4 = 0$
$A_3 = 0$	$B_3 = 0$	$S_3 = 0$	$C_3 = 0$
$A_2 = 0$	$B_2 = 0$	$S_2 = 0$	$C_2 = 0$
$A_1 = 0$	$B_1 = 0$	$S_1 = 0$	$C_1 = 0$

$S_{16} = 0$

$C_{16} = 0$

16 bit parallel adder using 4 4-bit parallel adder

$A_{10} = 0$	$B_{10} = 0$	$S_{10} = 0$	$C_{10} = 0$	
$A_9 = 0$	$B_9 = 0$	$S_9 = 0$	$C_9 = 0$	
$A_8 = 0$	$B_8 = 0$	$S_8 = 0$	$C_8 = 0$	
$A_7 = 0$	$B_7 = 0$	$S_7 = 0$	$C_7 = 0$	
$A_6 = 0$	$B_6 = 0$	$S_6 = 0$	$C_6 = 0$	
$A_5 = 0$	$B_5 = 0$	$S_5 = 0$	$C_5 = 0$	
$A_4 = 0$	$B_4 = 0$	$S_4 = 1$	$C_4 = 0$	$C_{in} = 0$
$A_3 = 0$	$B_3 = 1$	$S_3 = 0$	$C_3 = 1$	
$A_2 = 1$	$B_2 = 0$	$S_2 = 0$	$C_2 = 1$	
$A_1 = 1$	$B_1 = 1$	$S_1 = 0$	$C_1 = 1$	

Procedure: i) Firstly we need to open the circuit maker (v6). on the device.


- ii) For inputs, we go to the device option and then browse the switches and take 33 switches \rightarrow 32 for inputs and 1 for Carry input.
- iii) We take 1 4 bit parallel adder from the find option and putting the IC no. - 74LS83.
- iv) For outputs, we go to the logic display button and take 17 LEDs \rightarrow 16 for sum output and 1 for Cout.

v) Then we connect all the circuit switches and LEDs to the 4 bit adders like \rightarrow 1 bit of input A and input B each to each of the 4 adders and then connect one cout to the cin of the 2nd one and continue this chain process.

vi) After the completion of the circuit we run the circuit and check the truth table.

Conclusion: By doing this experiment, we got to know about the working of 16 bit-parallel adder and how to make it with the help of four 4-bit parallel adder.

Curr
18/9/23

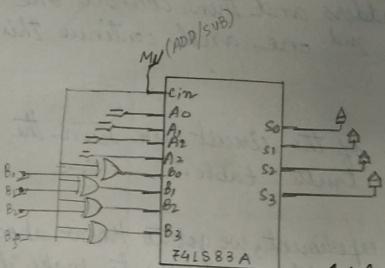

1 bit binary
Adder Subtractor

Experimental Result

INPUT								OUTPUT						
M	Cin	A ₀	A ₁	A ₂	A ₃	B ₀	B ₁	B ₂	B ₃	Cout	S ₀	S ₁	S ₂	S ₃
0	0	1	0	1	1	1	0	1	1	0	1	0	0	1
1	1	1	0	1	1	1	0	1	1	0	1	0	0	0

Experiment-8

Topic: Design an Adder Subtractor Composite unit and verify addition and subtraction.

PIONEER®

Page: 39

Date: / /

1-Bit Binary Adder-Subtractor

Theory: In Digital Circuits, A Binary - Adder - Subtractor is capable of both the addition and subtraction of binary numbers in one circuit itself. The operation is performed by depending on the binary value of the controlled signal holds. It is one of the components of the ALU.

Let consider two 4-bit Binary numbers A and B as inputs to the digital circuit.

A₀ A₁ A₂ A₃ for A

B₀ B₁ B₂ B₃ for B

The circuit consists of 4 full adders. Since, we are performing operations on 4-bit numbers.

The Mode (M) input controls the operations of the circuit.

Conditions for Working:

- 1) When M=0, circuit becomes an adder and operates (A+B)
- 2) When M=1, circuit becomes a subtractor and operates (A-B)

Procedure:

- i) Firstly, we need to open the circuit maker (v6) in our device.
- ii) For inputs, we go to the device option and then browse the switches option and place it on screen.
- iii) Then we need the 4 bit adder subtractor, i.e., IC - 74LS83. which has ~~8~~ 9 inputs and $A_0, A_1, A_2, A_3, B_0, B_1, B_2, B_3$ as inputs and Cin is connected to node (switch).
- iv) For output, we go to logic display option and take the LEDs as our display and place it on screen.
- v) After this we connect all the switches and LEDs and join them to the IC.
- vi) Then we run our circuit and verify our desired results.

Conclusion: In this experiment, we design 4-bit adder subtractor and get to know about how it works and gather knowledge. We also checked and verify our results.

| Sum | | A₁ | | A₂ | | A₃ | | A₄ | | A₅ | | A₆ | | A₇ | | A₈ | | A₉ | | A₁₀ | | A₁₁ | | A₁₂ | | A₁₃ | | A₁₄ | | A₁₅ | | A₁₆ | | A₁₇ | | A₁₈ | | A₁₉ | | A₂₀ | | A₂₁ | | A₂₂ | | A₂₃ | | A₂₄ | | A₂₅ | | A₂₆ | | A₂₇ | | A₂₈ | | A₂₉ | | A₃₀ | | A₃₁ | | A₃₂ | | A₃₃ | | A₃₄ | | A₃₅ | | A₃₆ | | A₃₇ | | A₃₈ | | A₃₉ | | A₄₀ | | A₄₁ | | A₄₂ | | A₄₃ | | A₄₄ | | A₄₅ | | A₄₆ | | A₄₇ | | A₄₈ | | A₄₉ | | A₅₀ | | A₅₁ | | A₅₂ | | A₅₃ | | A₅₄ | | A₅₅ | | A₅₆ | | A₅₇ | | A₅₈ | | A₅₉ | | A₆₀ | | A₆₁ | | A₆₂ | | A₆₃ | | A₆₄ | | A₆₅ | | A₆₆ | | A₆₇ | | A₆₈ | | A₆₉ | | A₇₀ | | A₇₁ | | A₇₂ | | A₇₃ | | A₇₄ | | A₇₅ | | A₇₆ | | A₇₇ | | A₇₈ | | A₇₉ | | A₈₀ | | A₈₁ | | A₈₂ | | A₈₃ | | A₈₄ | | A₈₅ | | A₈₆ | | A₈₇ | | A₈₈ | | A₈₉ | | A₉₀ | | A₉₁ | | A₉₂ | | A₉₃ | | A₉₄ | | A₉₅ | | A₉₆ | | A₉₇ | | A₉₈ | | A₉₉ | | A₁₀₀ | | A₁₀₁ | | A₁₀₂ | | A₁₀₃ | | A₁₀₄ | | A₁₀₅ | | A₁₀₆ | | A₁₀₇ | | A₁₀₈ | | A₁₀₉ | | A₁₁₀ | | A₁₁₁ | | A₁₁₂ | | A₁₁₃ | | A₁₁₄ | | A₁₁₅ | | A₁₁₆ | | A₁₁₇ | | A₁₁₈ | | A₁₁₉ | | A₁₂₀ | | A₁₂₁ | | A₁₂₂ | | A₁₂₃ | | A₁₂₄ | | A₁₂₅ | | A₁₂₆ | | A₁₂₇ | | A₁₂₈ | | A₁₂₉ | | A₁₃₀ | | A₁₃₁ | | A₁₃₂ | | A₁₃₃ | | A₁₃₄ | | A₁₃₅ | | A₁₃₆ | | A₁₃₇ | | A₁₃₈ | | A₁₃₉ | | A₁₄₀ | | A₁₄₁ | | A₁₄₂ | | A₁₄₃ | | A₁₄₄ | | A₁₄₅ | | A₁₄₆ | | A₁₄₇ | | A₁₄₈ | | A₁₄₉ | | A₁₅₀ | | A₁₅₁ | | A₁₅₂ | | A₁₅₃ | | A₁₅₄ | | A₁₅₅ | | A₁₅₆ | | A₁₅₇ | | A₁₅₈ | | A₁₅₉ | | A₁₆₀ | | A₁₆₁ | | A₁₆₂ | | A₁₆₃ | | A₁₆₄ | | A₁₆₅ | | A₁₆₆ | | A₁₆₇ | | A₁₆₈ | | A₁₆₉ | | A₁₇₀ | | A₁₇₁ | | A₁₇₂ | | A₁₇₃ | | A₁₇₄ | | A₁₇₅ | | A₁₇₆ | | A₁₇₇ | | A₁₇₈ | | A₁₇₉ | | A₁₈₀ | | A₁₈₁ | | A₁₈₂ | | A₁₈₃ | | A₁₈₄ | | A₁₈₅ | | A₁₈₆ | | A₁₈₇ | | A₁₈₈ | | A₁₈₉ | | A₁₉₀ | | A₁₉₁ | | A₁₉₂ | | A₁₉₃ | | A₁₉₄ | | A₁₉₅ | | A₁₉₆ | | A₁₉₇ | | A₁₉₈ | | A₁₉₉ | | A₂₀₀ | | A₂₀₁ | | A₂₀₂ | | A₂₀₃ | | A₂₀₄ | | A₂₀₅ | | A₂₀₆ | | A₂₀₇ | | A₂₀₈ | | A₂₀₉ | | A₂₁₀ | | A₂₁₁ | | A₂₁₂ | | A₂₁₃ | | A₂₁₄ | | A₂₁₅ | | A₂₁₆ | | A₂₁₇ | | A₂₁₈ | | A₂₁₉ | | A₂₂₀ | | A₂₂₁ | | A₂₂₂ | | A₂₂₃ | | A₂₂₄ | | A₂₂₅ | | A₂₂₆ | | A₂₂₇ | | A₂₂₈ | | A₂₂₉ | | A₂₃₀ | | A₂₃₁ | | A₂₃₂ | | A₂₃₃ | | A₂₃₄ | | A₂₃₅ | | A₂₃₆ | | A₂₃₇ | | A₂₃₈ | | A₂₃₉ | | A₂₄₀ | | A₂₄₁ | | A₂₄₂ | | A₂₄₃ | | A₂₄₄ | | A₂₄₅ | | A₂₄₆ | | A₂₄₇ | | A₂₄₈ | | A₂₄₉ | | A₂₅₀ | | A₂₅₁ | | A₂₅₂ | | A₂₅₃ | | A₂₅₄ | | A₂₅₅ | | A₂₅₆ | | A₂₅₇ | | A₂₅₈ | | A₂₅₉ | | A₂₆₀ | | A₂₆₁ | | A₂₆₂ | | A₂₆₃ | | A₂₆₄ | | A₂₆₅ | | A₂₆₆ | | A₂₆₇ | | A₂₆₈ | | A₂₆₉ | | A₂₇₀ | | A₂₇₁ | | A₂₇₂ | | A₂₇₃ | | A₂₇₄ | | A₂₇₅ | | A₂₇₆ | | A₂₇₇ | | A₂₇₈ | | A₂₇₉ | | A₂₈₀ | | A₂₈₁ | | A₂₈₂ | | A₂₈₃ | | A₂₈₄ | | A₂₈₅ | | A₂₈₆ | | A₂₈₇ | | A₂₈₈ | | A₂₈₉ | | A₂₉₀ | | A₂₉₁ | | A₂₉₂ | | A₂₉₃ | | A₂₉₄ | | A₂₉₅ | | A₂₉₆ | | A₂₉₇ | | A₂₉₈ | | A₂₉₉ | | A₃₀₀ | | A₃₀₁ | | A₃₀₂ | | A₃₀₃ | | A₃₀₄ | | A₃₀₅ | | A₃₀₆ | | A₃₀₇ | | A₃₀₈ | | A₃₀₉ | | A₃₁₀ | | A₃₁₁ | | A₃₁₂ | | A₃₁₃ | | A₃₁₄ | | A₃₁₅ | | A₃₁₆ | | A₃₁₇ | | A₃₁₈ | | A₃₁₉ | | A₃₂₀ | | A₃₂₁ | | A₃₂₂ | | A₃₂₃ | | A₃₂₄ | | A₃₂₅ | | A₃₂₆ | | A₃₂₇ | | A₃₂₈ | | A₃₂₉ | | A₃₃₀ | | A₃₃₁ | | A₃₃₂ | | A₃₃₃ | | A₃₃₄ | | A₃₃₅ | | A₃₃₆ | | A₃₃₇ | | A₃₃₈ | | A₃₃₉ | | A₃₄₀ | | A₃₄₁ | | A₃₄₂ | | A₃₄₃ | | A₃₄₄ | | A₃₄₅ | | A₃₄₆ | | A₃₄₇ | | A₃₄₈ | | A₃₄₉ | | A₃₅₀ | | A₃₅₁ | | A₃₅₂ | | A₃₅₃ | | A₃₅₄ | | A₃₅₅ | | A₃₅₆ | | A₃₅₇ | | A₃₅₈ | | A₃₅₉ | | A₃₆₀ | | A₃₆₁ | | A₃₆₂ | | A₃₆₃ | | A₃₆₄ | | A₃₆₅ | | A₃₆₆ | | A₃₆₇ | | A₃₆₈ | | A₃₆₉ | | A₃₇₀ | | A₃₇₁ | | A₃₇₂ | | A₃₇₃ | | A₃₇₄ | | A₃₇₅ | | A₃₇₆ | | A₃₇₇ | | A₃₇₈ | | A₃₇₉ | | A₃₈₀ | | A₃₈₁ | | A₃₈₂ | | A₃₈₃ | | A₃₈₄ | | A₃₈₅ | | A₃₈₆ | | A₃₈₇ | | A₃₈₈ | | A₃₈₉ | | A₃₉₀ | | A₃₉₁ | | A₃₉₂ | | A₃₉₃ | | A₃₉₄ | | A₃₉₅ | | A₃₉₆ | | A₃₉₇ | | A₃₉₈ | | A₃₉₉ | | A₄₀₀ | | A₄₀₁ | | A₄₀₂ | | A₄₀₃ | | A₄₀₄ | | A₄₀₅ | | A₄₀₆ | | A₄₀₇ | | A₄₀₈ | | A₄₀₉ | | A₄₁₀ | | A₄₁₁ | | A₄₁₂ | | A₄₁₃ | | A₄₁₄ | | A₄₁₅ | | A₄₁₆ | | A₄₁₇ | | A₄₁₈ | | A₄₁₉ | | A₄₂₀ | | A₄₂₁ | | A₄₂₂ | | A₄₂₃ | | A₄₂₄ | | A₄₂₅ | | A₄₂₆ | | A₄₂₇ | | A₄₂₈ | | A₄₂₉ | | A₄₃₀ | | A₄₃₁ | | A₄₃₂ | | A₄₃₃ | | A₄₃₄ | | A₄₃₅ | | A₄₃₆ | | A₄₃₇ | | A₄₃₈ | | A₄₃₉ | | A₄₄₀ | | A₄₄₁ | | A₄₄₂ | | A₄₄₃ | | A₄₄₄ | | A₄₄₅ | | A₄₄₆ | | A₄₄₇ | | A₄₄₈ | | A₄₄₉ | | A₄₅₀ | | A₄₅₁ | | A₄₅₂ | | A₄₅₃ | | A₄₅₄ | | A₄₅₅ | | A₄₅₆ | | A₄₅₇ | | A₄₅₈ | | A₄₅₉ | | A₄₆₀ | | A₄₆₁ | | A₄₆₂ | | A₄₆₃ | | A₄₆₄ | | A₄₆₅ | | A₄₆₆ | | A₄₆₇ | | A₄₆₈ | | A₄₆₉ | | A₄₇₀ | | A₄₇₁ | | A₄₇₂ | | A₄₇₃ | | A₄₇₄ | | A₄₇₅ | | A₄₇₆ | | A₄₇₇ | | A₄₇₈ | | A₄₇₉ | | A₄₈₀ | | A₄₈₁ | | A₄₈₂ | | A₄₈₃ | | A₄₈₄ | | A₄₈₅ | | A₄₈₆ | | A₄₈₇ | | A₄₈₈ | | A₄₈₉ | | A₄₉₀ | | A₄₉₁ | | A₄₉₂ | | A₄₉₃ | | A₄₉₄ | | A₄₉₅ | | A₄₉₆ | | A₄₉₇ | | A₄₉₈ | | A₄₉₉ | | A₅₀₀ | | A₅₀₁ | | A₅₀₂ | | A₅₀₃ | | A₅₀₄ | | A₅₀₅ | | A₅₀₆ | | A₅₀₇ | | A₅₀₈ | | A₅₀₉ | | A₅₁₀ | | A₅₁₁ | | A₅₁₂ | | A₅₁₃ | | A₅₁₄ | | A₅₁₅ | | A₅₁₆ | | A₅₁₇ | | A₅₁₈ | | A₅₁₉ | | A₅₂₀ | | A₅₂₁ | | A₅₂₂ | | A₅₂₃ | | A₅₂₄ | | A₅₂₅ | | A₅₂₆ | | A₅₂₇ | | A₅₂₈ | | A₅₂₉ | | A₅₃₀ | | A₅₃₁ | | A₅₃₂ | | A₅₃₃ | | A₅₃₄ | | A₅₃₅ | | A₅₃₆ | | A₅₃₇ | | A₅₃₈ | | A₅₃₉ | | A₅₄₀ | | A₅₄₁ | | A₅₄₂ | | A₅₄₃ | | A₅₄₄ | | A₅₄₅ | | A₅₄₆ | | A₅₄₇ | | A₅₄₈ | | A₅₄₉ | | A₅₅₀ | | A₅₅₁ | | A₅₅₂ | | A₅₅₃ | | A₅₅₄ | | A₅₅₅ | | A₅₅₆ | | A₅₅₇ | | A₅₅₈ | | A₅₅₉ | | A₅₆₀ | | A₅₆₁ | | A₅₆₂ | | A₅₆₃ | | A₅₆₄ | | A₅₆₅ | | A₅₆₆ | | A₅₆₇ | | A₅₆₈ | | A₅₆₉ | | A₅₇₀ | | A₅₇₁ | | A₅₇₂ | | A₅₇₃ | | A₅₇₄ | | A₅₇₅ | | A₅₇₆ | | A₅₇₇ | | A₅₇₈ | | A₅₇₉ | | A₅₈₀ | | A₅₈₁ | | A₅₈₂ | | A₅₈₃ | | A₅₈₄ | | A₅₈₅ | | A₅₈₆ | | A₅₈₇ | | A₅₈₈ | | A₅₈₉ | | A₅₉₀ | | A₅₉₁ | | A₅₉₂ | | A₅₉₃ | | A₅₉₄ | | A₅₉₅ | | A₅₉₆ | | A₅₉₇ | | A₅₉₈ | | A₅₉₉ | | A₆₀₀ | | A₆₀₁ | | A₆₀₂ | | A₆₀₃ | | A₆₀₄ | | A₆₀₅ | | A₆₀₆ | | A₆₀₇ | | A₆₀₈ | | A₆₀₉ | | A₆₁₀ | | A₆₁₁ | | A₆₁₂ | | A₆₁₃ | | A₆₁₄ | | A₆₁₅ | | A₆₁₆ | | A₆₁₇ | | A₆₁₈ | | A₆₁₉ | | A₆₂₀ | | A₆₂₁ | | A₆₂₂ | | A₆₂₃ | | A₆₂₄ | | A₆₂₅ | | A₆₂₆ | | A₆₂₇ | | A₆₂₈ | | A₆₂₉ | | A₆₃₀ | | A₆₃₁ | | A₆₃₂ | | A₆₃₃ | | A₆₃₄ | | A₆₃₅ | | A₆₃₆ | | A₆₃₇ | | A₆₃₈ | | A₆₃₉ | | A₆₄₀ | | A₆₄₁ | | A₆₄₂ | | A₆₄₃ | | A₆₄₄ | | A₆₄₅ | | A₆₄₆ | | A₆₄₇ | | A₆₄₈ | | A₆₄₉ | | A₆₅₀ | | A₆₅₁ | | A₆₅₂ | | A₆₅₃ | | A₆₅₄ | | A₆₅₅ | | A₆₅₆ | | A₆₅₇ | | A₆₅₈ | | A₆₅₉ | | A₆₆₀ | | A₆₆₁ | | A₆₆₂ | | A₆₆₃ | | A₆₆₄ | | A₆₆₅ | | A₆₆₆ | | A₆₆₇ | | A₆₆₈ | | A₆₆₉ | | A₆₇₀ | | A₆₇₁ | | A₆₇₂ | | A₆₇₃ | | A₆₇₄ | | A₆₇₅ | | A₆₇₆ | | A₆₇₇ | | A₆₇₈ | | A₆₇₉ | | A₆₈₀ | | A₆₈₁ | | A₆₈₂ | | A₆₈₃ | | A₆₈₄ | | A₆₈₅ | | A₆₈₆ | | A₆₈₇ | | A₆₈₈ | | A₆₈₉ | | A₆₉₀ | | A₆₉₁ | | A₆₉₂ | | A₆₉₃ | | A₆₉₄ | | A₆₉₅ | | A₆₉₆ | | A₆₉₇ | | A₆₉₈ | | A₆₉₉ | | A₇₀₀ | | A₇₀₁ | | A₇₀₂ | | A₇₀₃ | | A₇₀₄ | | A₇₀₅ | | A₇₀₆ | | A₇₀₇ | | A₇₀₈ | | A₇₀₉ | | A₇₁₀ | | A₇₁₁ | | A₇₁₂ | | A₇₁₃ | | A₇₁₄ | | A₇₁₅ | | A₇₁₆ | | A₇₁₇ | | A₇₁₈ | | A₇₁₉ | | A₇₂₀ | | A₇₂₁ | | A₇₂₂ | | A₇₂₃ | | A₇₂₄ | | A₇₂₅ | | A₇₂₆ | | A₇₂₇ | | A₇₂₈ | | A₇₂₉ | | A₇₃₀ | | A₇₃₁ | | A₇₃₂ | |
<th colspan="2
| --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- | --- |

Truth Table of Full Adder:


INPUT			OUTPUT	
A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Topic

PRACTICE
Page 42

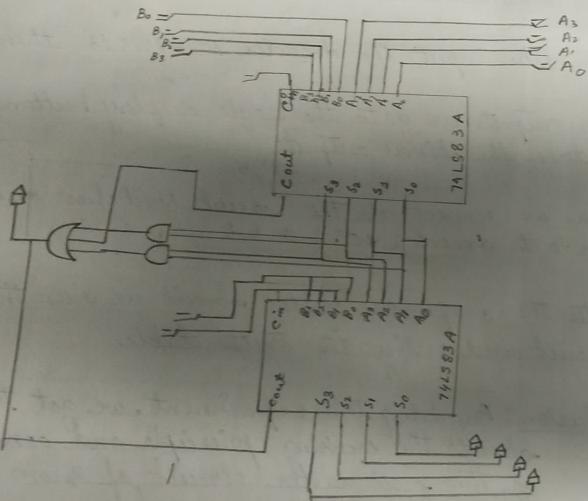- ii) For inputs, we go to the device option and then browse the switches. and
- iii) We take input the decoder IC - 74LS13 then
- iv) For outputs, we go to the logic display button and take the LEDs as outputs
- v) Then we connect all the circuit switches and LEDs to the decoder IC.
- vi) After the completion of the circuit we run the circuit and verify the truth table.

Conclusion: By doing this experiment, we got to know about the working principle and connection of the full adder circuit of sum and carry.



BCD Adder

Experiment - 10

Topic: Design a BCD adder using circuit maker (VG).

PIONEER®
Page 43
Date:

BCD Adder

BCD stands for binary coded decimal. It is used to perform the addition of BCD numbers. A BCD digit can have any of ten possible four-bit representations. Computers to Calculators which carry out the arithmetic operations directly in the decimal number system represent the numbers in BCD form.

Suppose, we have two 4-bit numbers A and B. The value of A and B can vary from 0 (0000) to 9 (1001) because we are considering decimal numbers.

The output will vary from 0 to 18 if we are not considering from the previous sum. But if we are considering the carry, then the maximum value of the output will be 19 ($1+9+9$). When we simply adding A and B, then we get the binary sum.

Example :

Input :
 $A = 0111 \quad B = 1000$

Output : $Y = 10101$

Explanation: We are adding A(7) and B(8). The value of binary sum will be 1111 (15) But the BCD sum will be 10101, where

Decimal	Binary Sum					BCD Sum				
	C'	S ₃ '	S ₂ '	S ₁ '	S ₀ '	C	S ₃	S ₂	S ₁	S ₀
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	1
2	0	0	0	1	0	0	0	0	1	0
3	0	0	0	1	1	0	0	0	1	1
4	0	0	1	0	0	0	0	1	0	0
5	0	0	1	0	1	0	0	1	0	1
6	0	0	1	1	0	0	0	1	1	0
7	0	0	1	1	1	0	0	1	1	1
8	0	1	0	0	0	0	1	0	0	0
9	0	1	0	0	1	0	1	0	0	1
10	0	1	0	1	0	1	0	0	1	0
11	0	1	0	1	1	1	0	0	1	1
12	0	1	1	0	0	1	0	1	0	0
13	0	1	1	0	1	1	0	1	0	1
14	0	1	1	1	0	1	0	1	1	0
15	0	1	1	1	1	1	0	1	1	1
16	1	0	0	0	0	1	0	0	0	0
17	1	0	0	0	1	1	0	0	0	1
18	1	0	0	1	0	1	1	0	1	0
19	1	0	0	1	1	1	1	0	1	1

7 is 0001 and 5 is 0101 in binary respectively

Procedures:

- Firstly, we need to open the circuit maker (v6) on the device.
- For inputs, we go to the device option and then browse the switches and get your desired ones.
- Then we take the 4-bit parallel adder from the find option and putting the IC No- 74LS83.
- For outputs, we go to the logic display button and take the LEDs as much as required.
- Then we connect all the switches and LEDs as to the adder and continue the chain process.
- After completing the circuit we run it and verify our results.

Conclusion: By doing this experiment, we get to know about the concept of BCD adder. If the sum of two nos is less than or equal to 9, then the value of BCD sum is same as the binary sum otherwise, they will differ by 6 (0110 in binary).